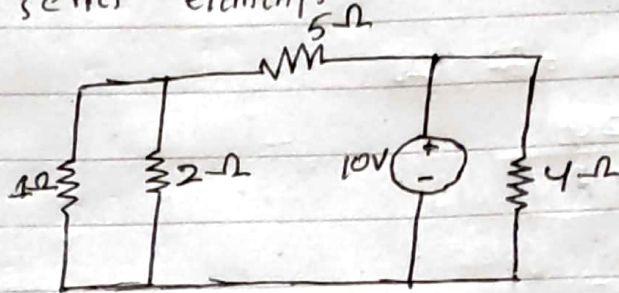


## Practice Problem (2-4):-

Identify the number of branches and nodes in given circuit. Also identify the parallel and series elements.



There are 5 elements in circuit, hence the circuit has 5 branches  $1\Omega$ ,  $2\Omega$ ,  $5\Omega$ ,  $10V$ ,  $4\Omega$ . The circuit has 3 nodes. The  $1\Omega$  and  $2\Omega$  resistors are in parallel. The  $4\Omega$  resistor and  $10V$  source are also in parallel.

## Practice problem (2-5):-


Find  $V_1$  and  $V_2$  in the given circuit.

solution

Applying KVL,

$$-32 + V_1 - (-8) - V_2 = 0$$
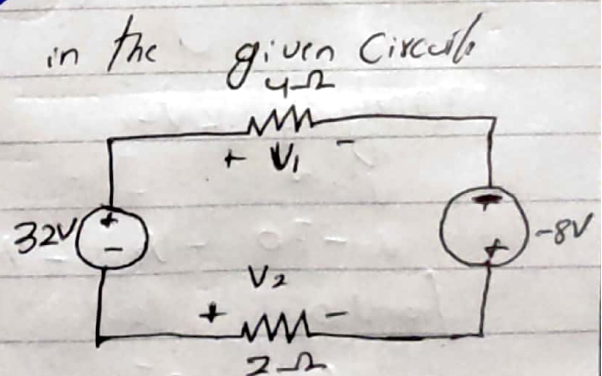
$$V_1 + 8 = 32 + V_2 \quad \text{--- (i)}$$



from ohm law,

$$V_1 = 4I$$

$$V_2 = -2I$$

eq (i) become

$$4I + 8 = 32 - 2I$$

$$6I = 24$$

$$I = 4A$$

$$= V_1 = 4I$$

$$V_1 = 4(4)$$

$$V_1 = 16V$$

$$= V_2 = -2I$$

$$V_2 = -2(4)$$


$$V_2 = -8V$$

### Practice problem (2-6):

find  $V_x$  and  $V_o$  in the given circuit

solution.

Applying KVL,

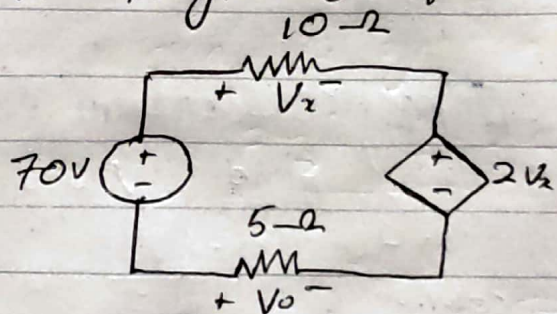

$$-70 + V_x + 2V_x - V_o = 0 \quad \text{--- (1)}$$

from ohm's law

$$V_x = 10I$$

$$V_o = -5I$$

eq (i) become.



$$-70 + 10I + 2(10I) - (-5I) = 0$$

$$-70 + 10I + 20I + 5I = 0$$

$$35I = 70$$

$$I = \frac{70}{35}$$

$$I = 2A$$

$$\therefore V_x = 10I$$

$$V_x = 10(2)$$

$$V_x = 20V$$

$$\therefore V_o = -5I$$

$$V_o = -5(2)$$


$$V_o = -10V$$

### Practic problem (2.7):-

find  $V_o$  and  $i_o$  in the given circuit.

solution.

Applying KCL.

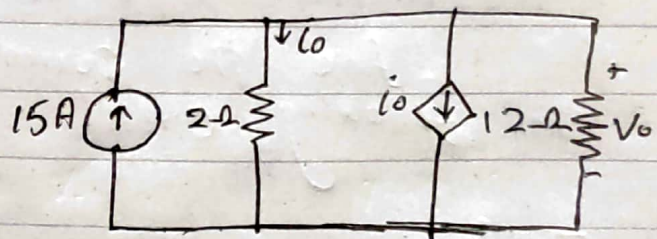

$$15 - i_o - i_o - \frac{V_o}{12} = 0$$

voltage is same so, from Ohm's law

$$V_o = 2i_o$$

$$(i) \text{ become } \Rightarrow 15 - i_o - i_o - \frac{2i_o}{12} = 0$$

$$15 - 2i_0 - \frac{2i_0}{6} = 0$$

$$\frac{90 - 12i_0 - i_0}{6} = 0$$

$$90 - 13i_0 = 0$$

$$90 = 13i_0$$

$$i_0 = 90/13$$

$$i_0 = 6.92 \text{ A}$$

$$V_0 = 2i_0$$

$$= 2(6.92)$$

$$V_0 = 13.84 \text{ V}$$

### Practice problem (2.8) =

find the current and voltages in the following circuit

To find:


$$V_1 = ? , I_1 = ?$$

$$V_2 = ? , I_2 = ?$$

$$V_3 = ? , I_3 = ?$$

solution

loop 1 according to KVL.

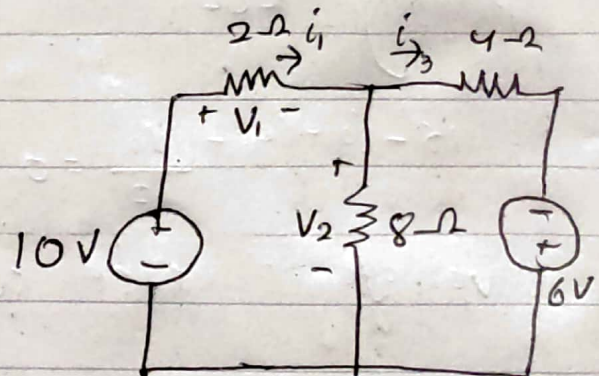



$$10 + V_1 + V_2 = 0 \quad \text{--- (i)}$$

from Ohm's law

$$V_1 = 2I_1, \quad V_2 = 8I_2$$

(i) become

$$-10 + 2I_1 + 8I_2 = 0$$

$$I_1 = \frac{10 - 8I_2}{2} \quad \text{--- (I)}$$

loop 2 according to KVL,

$$-V_2 + V_3 - 6 = 0 \quad \text{--- (ii)}$$

from Ohm's law

$$V_2 = 8I_2, \quad V_3 = 4I_3$$

(ii) becomes

$$-8I_2 + 4I_3 - 6 = 0$$

$$I_3 = \frac{6 + 8I_2}{4} \quad \text{--- (II)}$$

According to KCL on node (a),

$$I_1 - I_2 - I_3 = 0$$

putting value of  $I_1$  and  $I_3$

$$\left( \frac{10 - 8I_2}{2} \right) - I_2 - \left( \frac{6 + 8I_2}{4} \right) = 0$$

$$5 - 4I_2 - I_2 - \left( \frac{3 + 4I_2}{2} \right) = 0$$

$$5 - 5I_2 - \left( \frac{3 + 4I_2}{2} \right) = 0$$

$$\frac{10 - 10I_2 - 3 - 4I_2}{2} = 0$$

$$\frac{7 - 14I_2}{2} = 0$$

$$\boxed{7 - 14I_2 = 0}$$

$$\boxed{I_2 = 500 \text{ mA}}$$

Putting  $I_2$  in (I),

$$I_1 = \frac{10 - 8(500 \times 10^{-3})}{2}$$

$$\boxed{I_1 = 3 \text{ A}}$$

Putting  $I_2$  in (II)

$$I_3 = \frac{6 + 8(500 \times 10^{-3})}{4}$$

$$\boxed{I_3 = 2.5 \text{ A}}$$

from Ohm's law

$$V_1 = 2I_1 = 2(3) = \boxed{6 \text{ V}}$$


$$V_2 = 8I_2 = 8(500 \times 10^{-3}) = \boxed{4 \text{ V}}$$

$$V_3 = 4I_3 = 4(2.5) = \boxed{10 \text{ V}}$$


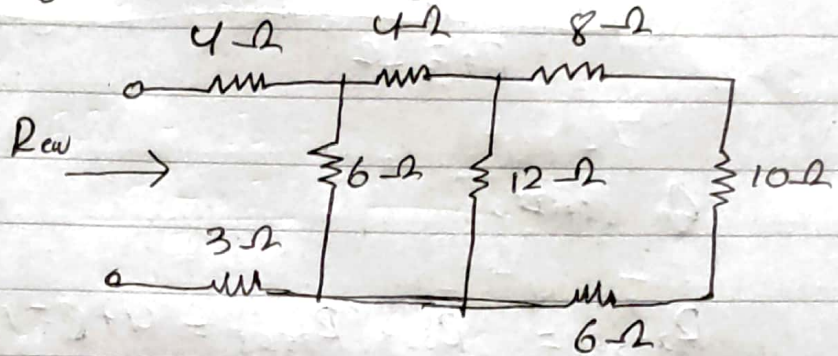
## Practice problem (2.9):


By combining resistors in given figure. find  $R_{eq}$



Solution,

4n series

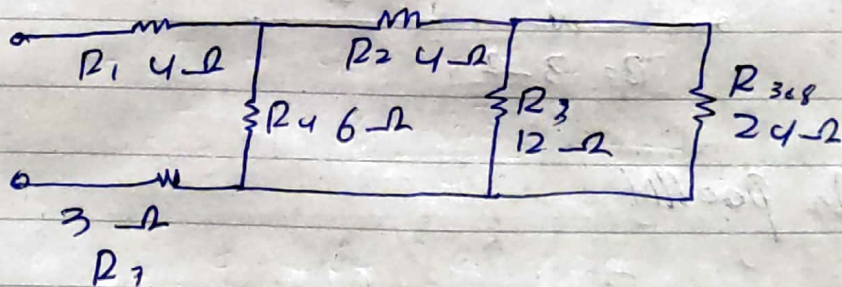
$$R_{368} = R_3 + R_6 + R_8 = 8 + 10 + 6 = 24 \Omega$$



4n parallel,


$$\frac{1}{R_{368}} = \frac{1}{R_3} + \frac{1}{368}$$

$$= R_{3568} = 8 \Omega$$

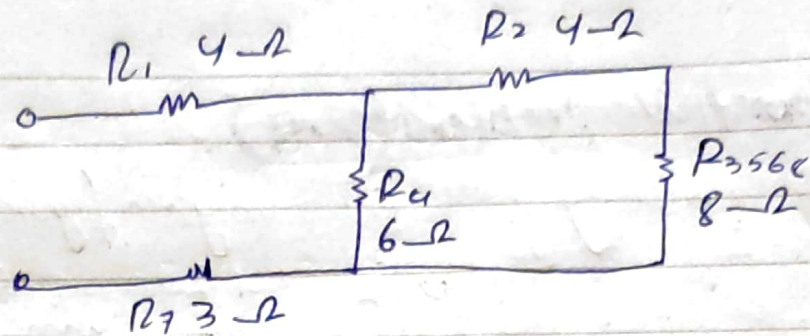

An series
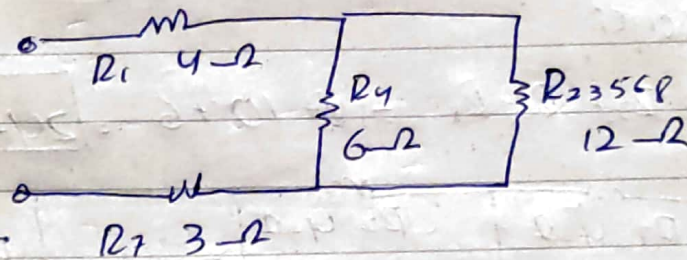
$$R_{23568} = R_2 + R_{3568} = 4 + 8 = 12 \Omega$$




An parallel

$$\begin{aligned} \frac{1}{R_{234568}} &= \frac{1}{R_4} + \frac{1}{R_{23568}} \\ &= \frac{1}{6} + \frac{1}{12} \end{aligned}$$

$$R_{234568} = 4 \Omega$$



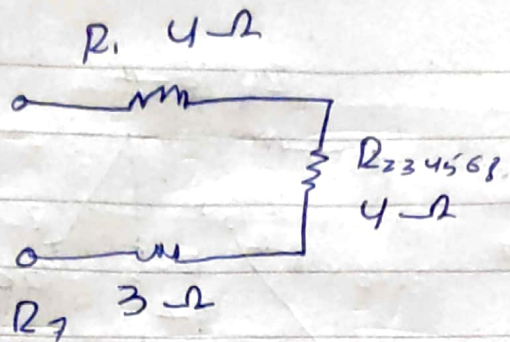

Ans.

$$R_{12345678} = R_{eq} = R_1 + R_{234568} + R_7$$


$$R_{eq} = 4 + 4 + 3 = \boxed{11\ \Omega}$$

### Practice problem (2-10).

Find  $R_{ab}$  for the given circuit.

solution.

In parallel

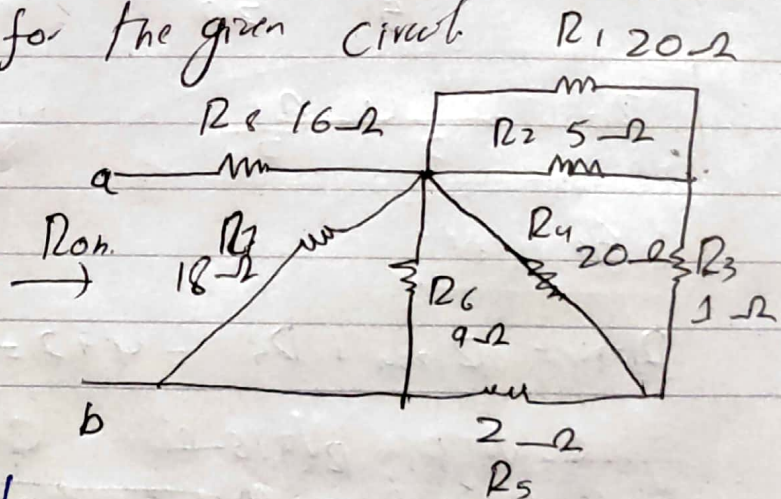

$$\frac{1}{R_{12}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{12}} = \frac{1}{20} + \frac{1}{5}$$

$$R_{12} = 4 \Omega$$

• 4 series

$$R_{123} = R_{12} + R_3 = 5 \Omega$$

4n parallel


$$\frac{1}{R_{1234}} = \frac{1}{R_{123}} + \frac{1}{R_4}$$

$$= \frac{1}{5} + \frac{1}{20}$$


$$R_{1234} = 4 \Omega$$

4n series
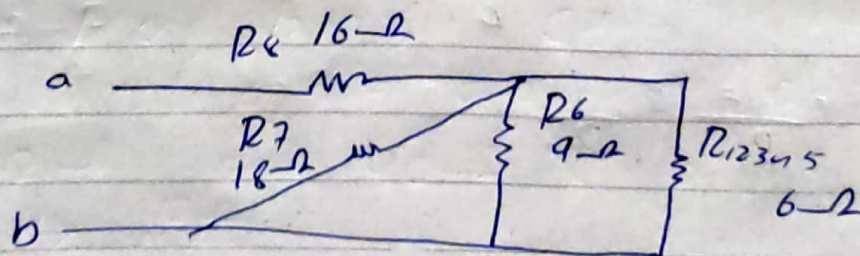
$$R_{12345} = R_{1234} + R_5 = 4 + 2 = 6 \Omega$$



4n parallel

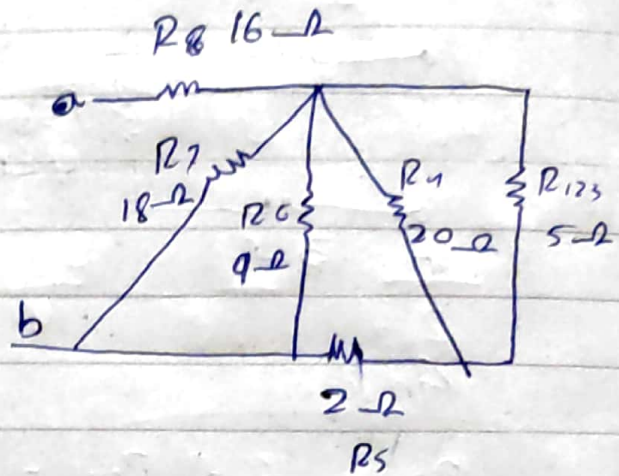




$$\frac{1}{R_{67}} = \frac{1}{R_7} + \frac{1}{R_6}$$

$$\frac{1}{R_{67}} = \frac{1}{18} + \frac{1}{9} \quad R_8 = 16\Omega$$

$$R_{67} = 6\Omega$$

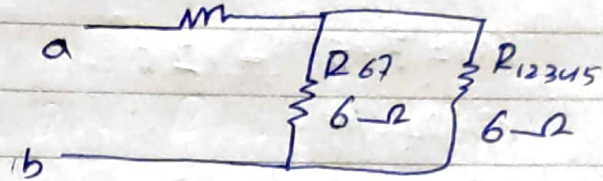

In parallel

$$\frac{1}{R_{1234567}} = \frac{1}{R_{67}} + \frac{1}{R_{12345}}$$

$$= \frac{1}{6} + \frac{1}{6}$$

$$R_{1234567} = 3\Omega$$

In series


$$R_{12345678} = R_{1234567} + R_8 = 3 + 16 = 19\Omega$$

**Practice Problem (2-11).**

Calculate  $G_{eq}$  in the given circuit

solution,

An parallel,

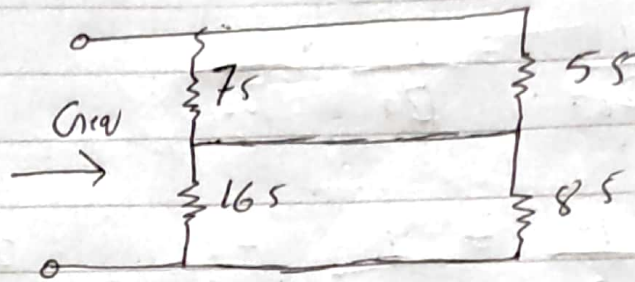

$$G_1 = 7 + 5 = 12S$$

An parallel

$$G_2 = 16 + 8 = 24S$$

An series,


$$\frac{1}{G_{eq}} = \frac{1}{G_1} + \frac{1}{G_2}$$

$$= \frac{1}{12} + \frac{1}{24}$$

$$G_{eq} = 8S$$
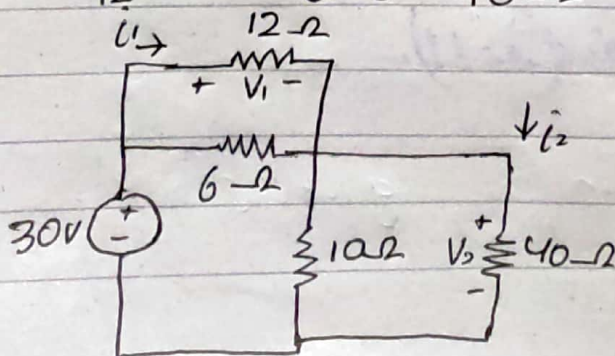
### Practive Problem:-(2.12)

find  $V_1$  and  $V_2$  in the circuit - Also calculate  $i_1$  and  $i_2$  and power dissipated in  $12\Omega$  and  $40\Omega$  resistor





To find,

$$\begin{aligned} V_1 = ? & , & V_2 = ? \\ i_1 = ? & , & i_2 = ? \\ P_{12} = ? & , & P_{40} = ? \end{aligned}$$

solution.

In parallel,

$$\frac{1}{R_1} = \frac{1}{12} + \frac{1}{6}$$


$$\frac{1}{R_1} = \frac{1}{4}$$

$$\boxed{R_1 = 4 \Omega}$$

In parallel,

$$\begin{aligned} \frac{1}{R_2} &= \frac{1}{10} + \frac{1}{40} \\ &= \frac{1}{8} \Omega \end{aligned}$$

$$\boxed{R_2 = 8 \Omega}$$

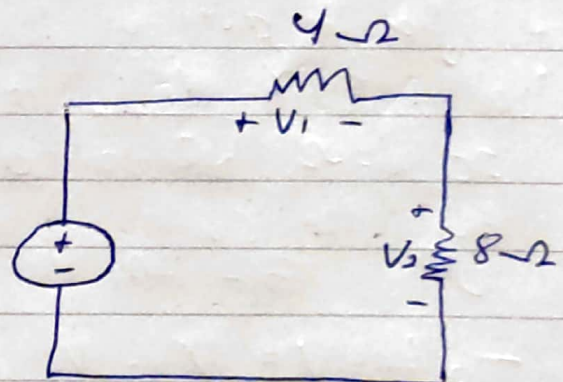

$$V_1 = \frac{(4)(30)}{4+8} = \boxed{10V} ; V_2 = \frac{(8)(30)}{8+4} = \boxed{20V}$$

from Ohm's law,

$$i_1 = \frac{V_1}{R} = \frac{10}{12} = \boxed{833.83 \text{ mA}}$$

$$i_2 = \frac{V_2}{R} = \frac{20}{40} = \boxed{500 \text{ mA}}$$

$$P_{12} = i_1 V_1 = (833.83 \times 10^{-3})(10)$$

$$\boxed{P_{12} = 8.33 \text{ W}}$$

$$P_{40} = i_2 V_2 = (800 \times 10^{-3})(20)$$

$$\boxed{P_{40} = 10 \text{ W}}$$

### Practise problem (12.13)-


for the given circuit. find (a)  $V_1$  and  $V_2$ ,  
 (b) power dissipated in  $3\text{-k}\Omega$  and  
 $20\text{-k}\Omega$  resistor and (c) power supplied  
 by the current source

To find,

a)  $V_1 = ?$  ,  $V_2 = ?$

b)  $P_3 = ?$  ,  $P_{15} = ?$

c)  $P = ?$

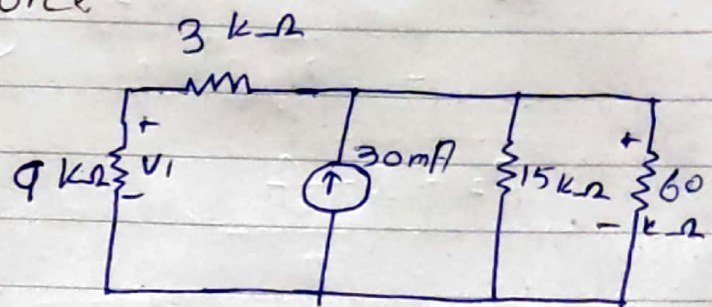



Solution

Applying KCL at node A.

$$30 = \frac{V_A}{3+9} + \frac{V_A}{15} + \frac{V_A}{60}$$

$$30 = \frac{5V_A + 4V_A + V_A}{60}$$

$$1800 = 10V_A$$

$$180 = V_A$$

Let

$$V_2 = V_A$$

$$\boxed{V_2 = 180V}$$

Applying Voltage divider Rule for  $V_1$ .

$$V_1 = \frac{R_1}{R_1 + R_2} \times V$$

$$= \frac{9}{9+3} \times 180$$

$$\boxed{V_1 = 135V}$$

for power :- at  $9k\Omega$  Resistor.

$$P_9 = \frac{V^2}{R_9}$$

$$P_9 = \frac{(135)^2}{9000}$$

$$P_9 = 2.025 \text{ watt}$$

at  $60 \text{ k}\Omega$  resistor

$$P_{60} = \frac{V_2^2}{R_{60}} = \frac{(180)^2}{60000}$$

$$P_{60} = 0.54 \text{ watt}$$

at  $15 \text{ k}\Omega$  resistor

$$P_{15} = \frac{V_2^2}{R_{15}} = \frac{180^2}{15000} = 2.16 \text{ watt}$$

at  $3 \text{ k}\Omega$  resistor

$$V = V_2 - V_1$$

$$= 180 - 135$$

$$V = 45 \text{ V}$$

$$P_3 = \frac{V^2}{R} = \frac{(45)^2}{3000}$$

$$P_3 = 0.675 \text{ watt}$$



power for whole circuit:

$$P = VI$$

$$P = (180) (30 \times 10^{-3})$$

$$P = 5.4 \text{ watt}$$